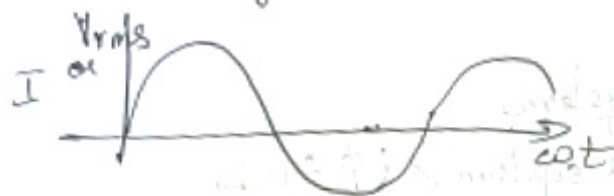


3 Phase Circuits

A system which generates single alternating voltage & current is termed as 'single phase system (1ϕ)'. It utilizes only one winding.







Phase diagram

$$V = V_m \sin \omega t$$

A three phase system (3ϕ) consists of three phases which are separate but identical windings are used. These windings are displaced electrically with a 120° phase shift.

These windings are shown below.

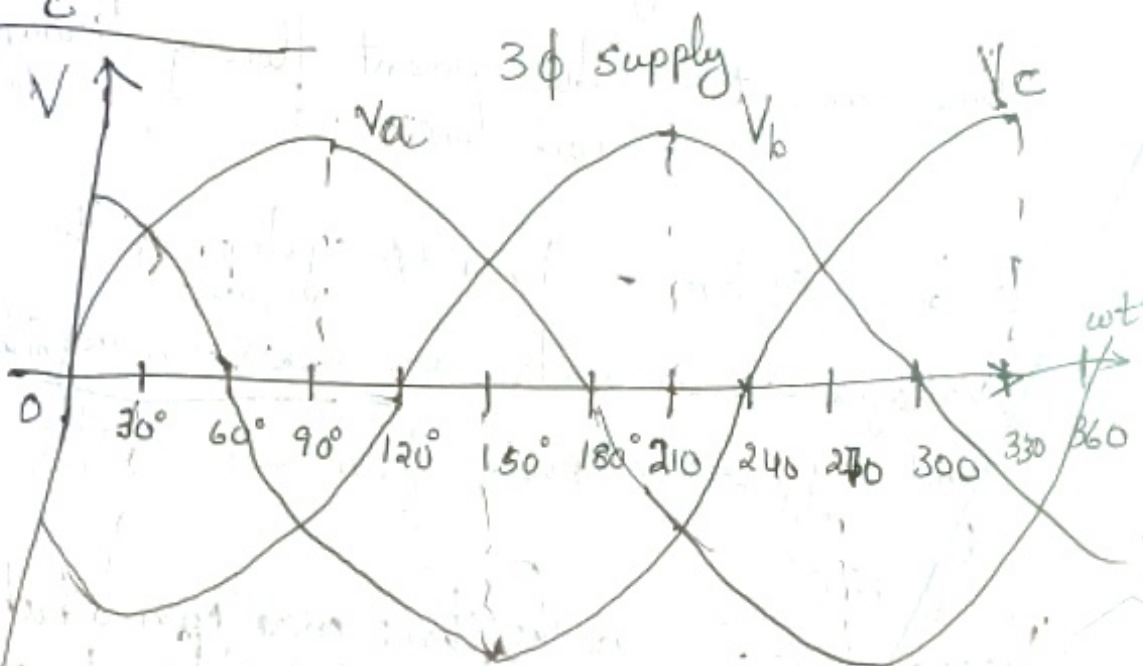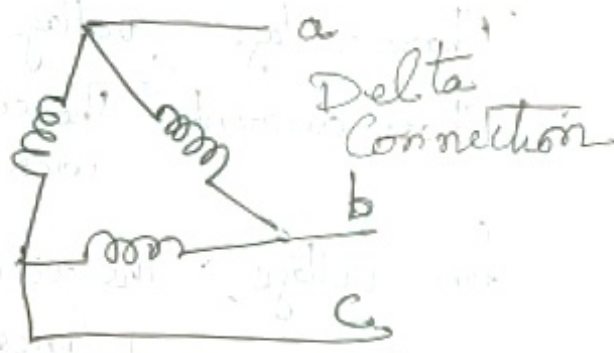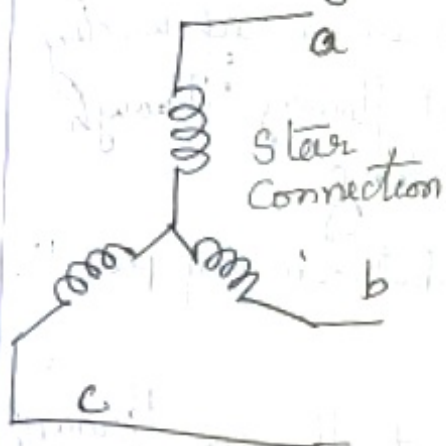

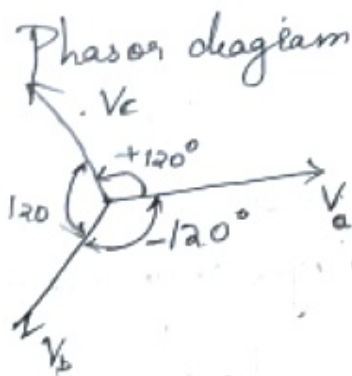

3 ϕ

Advantages of 3 ϕ system

- * The output of the 3 ϕ system > 1 ϕ system
- * Transmission & distribution costs are low

Disadvantages

- * 6 conductors required

Basic Terminology

Phase voltage - voltage induced in each winding

Phase current - The current flowing through each winding.

line voltage - The voltage between any pair of lines

line current - The current flowing through each line

Balanced system - In a 3 ϕ system if the

voltages & currents are equal in magnitude and differs in phase from one another by 120° .


Phase sequence - It is the time order in which the voltages pass through their respective max values

Types of connections of 3 ϕ $\angle 120^\circ$ $V_{cn} = V_p \angle +120^\circ$


Star connection | Balanced \rightarrow (only case considered here in class)

Delta connection | Unbalanced

3 ϕ Source (Star connected)

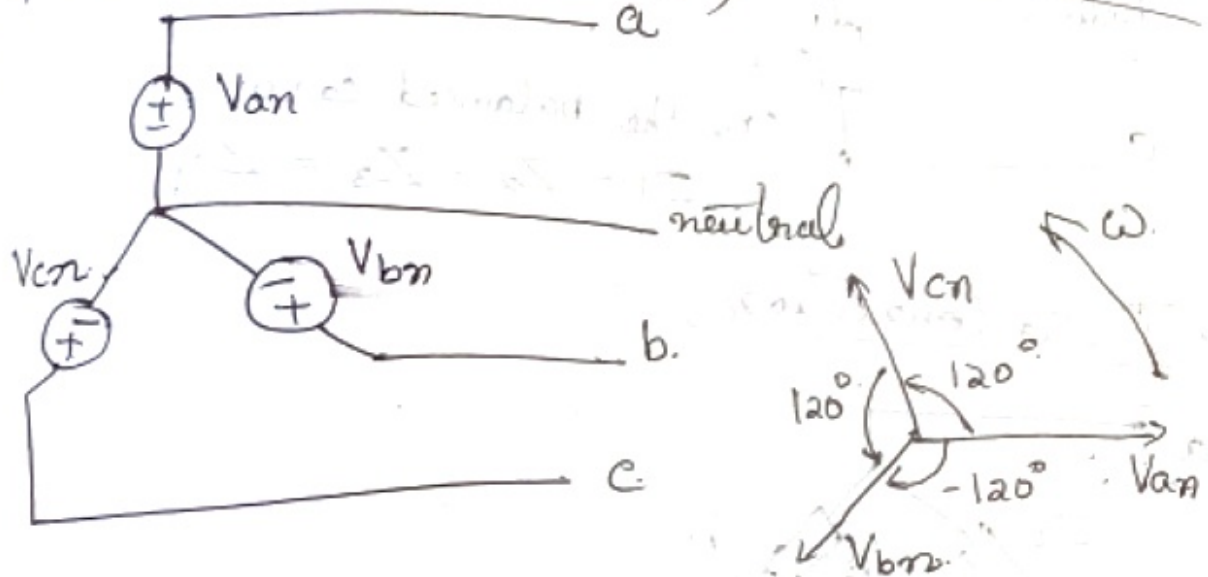

3 ϕ Source (Delta Connected)

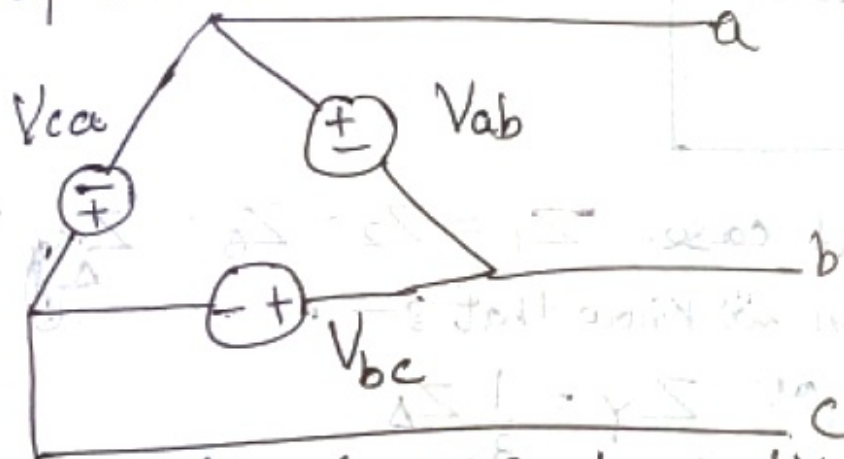

In the balanced case, $|V_{an}| = |V_{bn}| = |V_{cn}| = V_p$


$V_{an} = V_p \angle 0^\circ$

$V_{bn} = V_p \angle -120^\circ$

$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$


$\left. \begin{array}{l} V_{an} \text{ leads} \\ V_{bn} \text{ leads} \\ V_{cn} \end{array} \right\}$

Phasor diagram

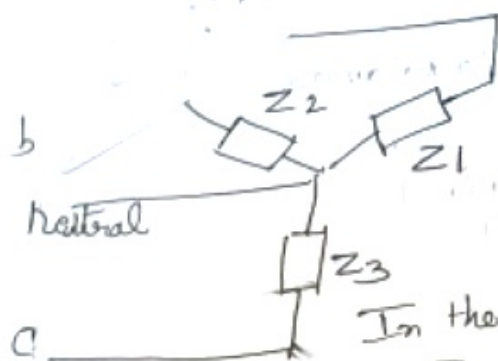

In the balanced case:
 $Z_1 = Z_2 = Z_3 = Z_Y$

Delta Connection

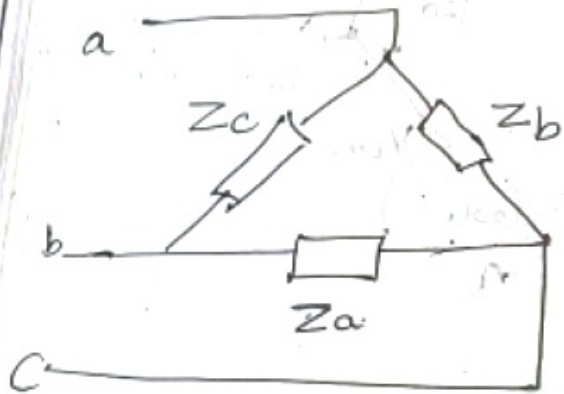


In the balanced case. $Z_1 = Z_2 = Z_3 = Z_Y$
 Also, by conversion we know that :-

$$Z_\Delta = 3Z_Y \text{ or } Z_Y = \frac{1}{3} Z_\Delta$$

Star Connection

Consider a balanced 4 wire Y-Y system

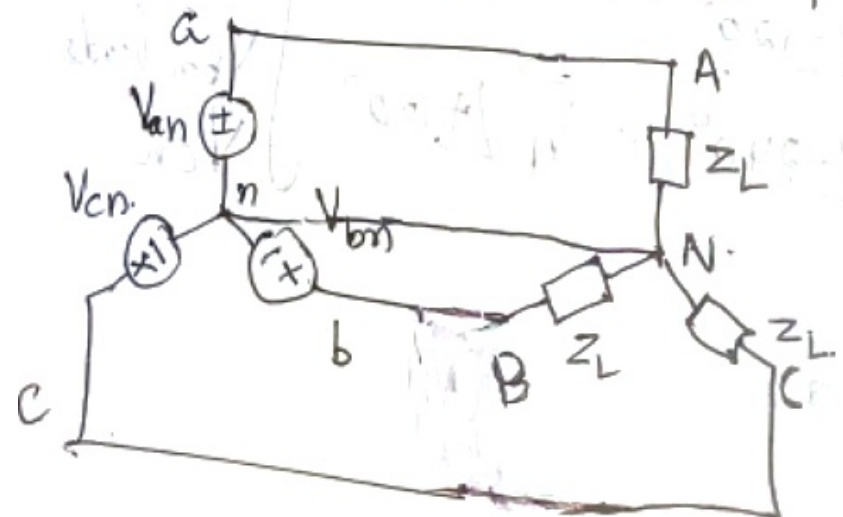

(mention Z_s & Z_L are small)

Phase Voltages (V_p)
 $V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$

Line Voltages (V_L)

$$V_{ab} = V_{an} + V_{nb} = V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ$$

$$= V_p \left(1 + \frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ$$

Similarly, $V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ$

$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ$

$$|V_L| = \sqrt{3} V_p$$

Applying KVL to each phase, we obtain line currents


$$I_a = \frac{V_{an} \angle 0^\circ}{Z_y} \quad I_b = \frac{V_{bn}}{Z_y} = \frac{V_{an} \angle -120^\circ}{Z_y} = I_a \angle -120^\circ$$

$$I_c = \frac{V_{cn}}{Z_y} = \frac{V_{an} \angle +120^\circ}{Z_y} = I_a \angle +120^\circ$$


$$I_n = I_a + I_b + I_c = I_a (1 + 1 \angle -120^\circ + 1 \angle +120^\circ)$$

$$I_n = I_a (0) = 0$$

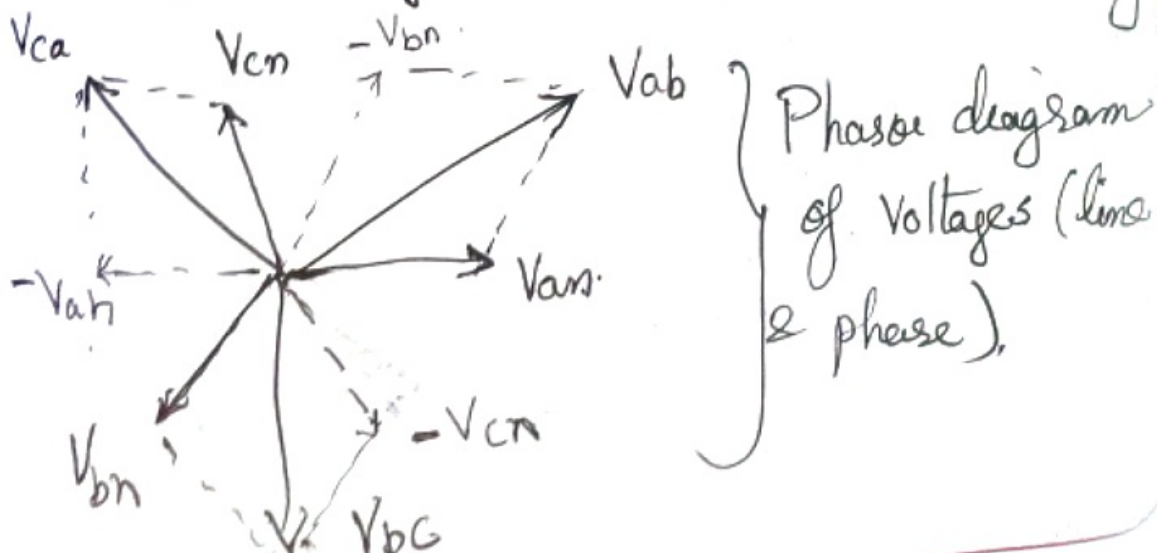Line current is the same as phase current, and presence of neutral wire is not mandatory



Balanced Δ - Δ connections

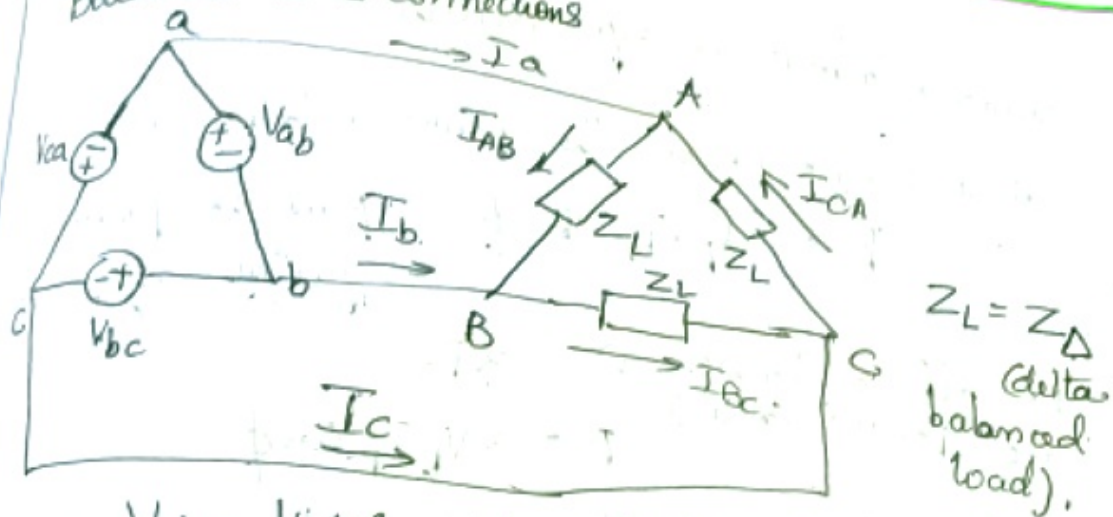

$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$
The line voltages are the same as phase voltages.

Phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}} \quad I_{BC} = \frac{V_{BC}}{Z_{\Delta}} = \frac{V_{bc}}{Z_{\Delta}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}} = \frac{V_{ca}}{Z_{\Delta}}$$

KCL at node A, B, C respectively gives us.

$$I_a = I_{AB} - I_{CA} = I_{AB} (1 - 1 \angle +120^\circ) = \sqrt{3} I_{AB} \angle -30^\circ$$

$$I_b = I_{BC} - I_{AB} = I_{AB} (1 \angle -120^\circ - 1) = \sqrt{3} I_{AB} \angle -150^\circ$$

$$I_c = I_{CA} - I_{BC} = I_{AB} (1 \angle +120^\circ - 1 \angle -120^\circ) = \sqrt{3} I_{AB} \angle 90^\circ$$

So $I_a = I_b = I_c = I_L$ (line current)

$$I_L = \sqrt{3} I_P$$