

# Basic Electrical and Electronics Engineering

## BEEE102L

### 3 phase systems numerical


**Dr. Sonam Shrivastava/ Assistant Professor (Sr.) /SELECT**

**LECTURE 10**

**Question: 3 Coils having resistance 10 ohms and 42mH are connected in (i) Y and (ii) Delta to a 415 V, 50 Hz 3- phase Supply. Calculate**

- a) Line and Phase voltages**
- b) Line and phase currents**
- c) Power consumed by load**  
**in both the cases.**

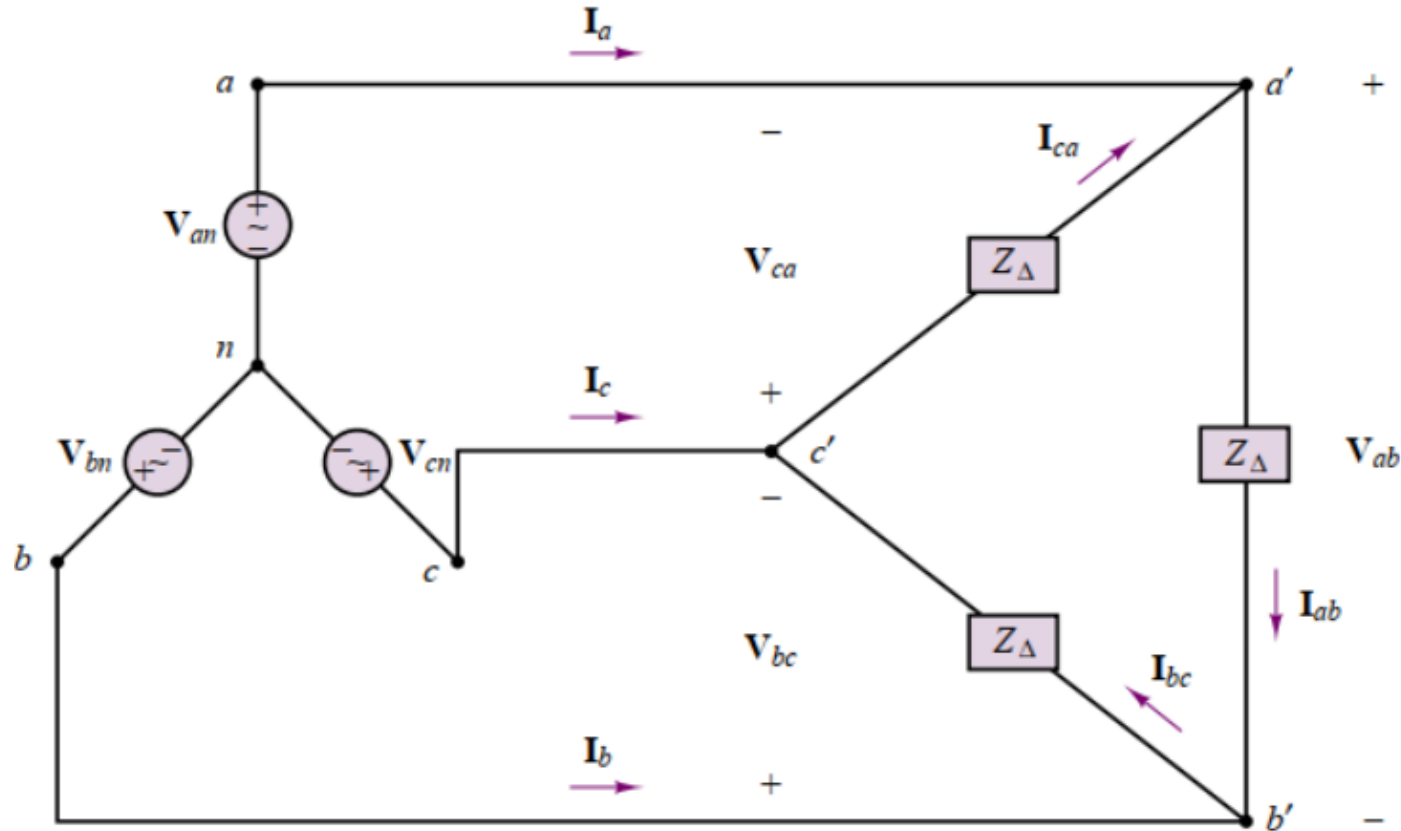**Question:: For the three phase system given where  $V_{an}=V_{bn}=V_{cn}=230$  V, 50 Hz , with phase impedance is  $30+40j$ . Find the following values: Phase voltages for load, Phase current in load , Supply current by each phase, Power factor, Total power consumed by load .**



$$V_p = V_{an} = V_{bn} = V_{cn} = 230 \text{ V, } 50 \text{ Hz}$$

$$V_L = \sqrt{3} V_p = \sqrt{3} \times 230 \text{ V} = 398.37 \text{ V}$$

(i) Phase voltage for load

$$V_p (\text{load}) = 398.37 \text{ V}$$

$$(ii) \quad I_p = \frac{V_p}{Z_p} = \frac{230}{\sqrt{30^2 + 40^2}} = 4.6 \text{ Amp.}$$

(iii) Supply current = line current of load

$$I_L = 4.6 \times \sqrt{3} = 7.967 \text{ Amp.}$$

$$(iv) \quad \cos \phi = \frac{R}{Z} = \frac{30}{\sqrt{30^2 + 40^2}} = 0.6$$

(v) Power consumed by load,


$$P = \sqrt{3} V_L I_L \cos \phi$$

$$P = \sqrt{3} \times 398.37 \times 7.967 \times 0.6$$


$$P = 8.298 \text{ kW}$$

**Calculate the current in three wire Y-Y System.**

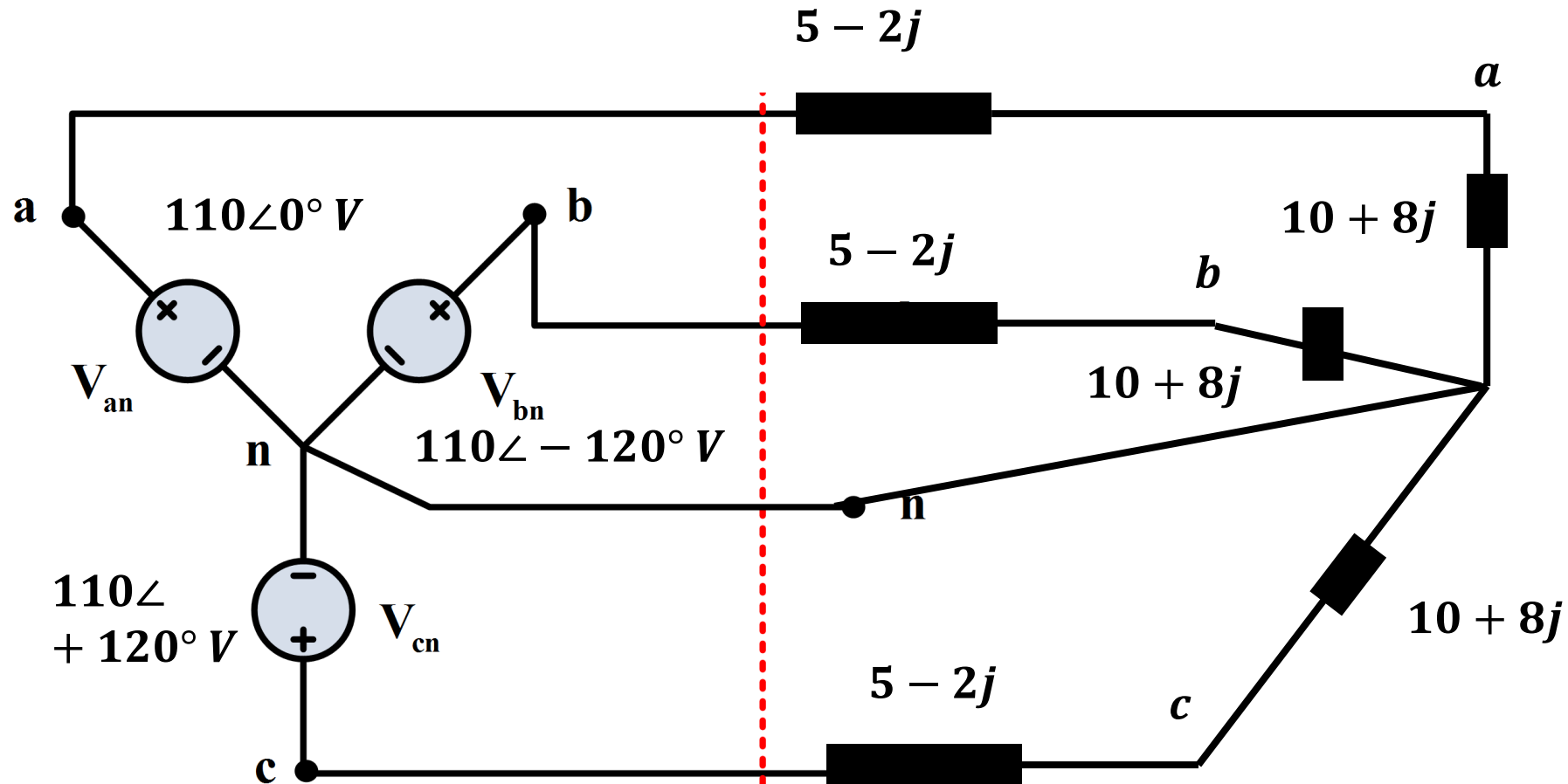- (i) Apparent power absorbed by source.**
- (ii) Apparent Power absorbed by load**
- (iii) Apparent Power absorbed by line**



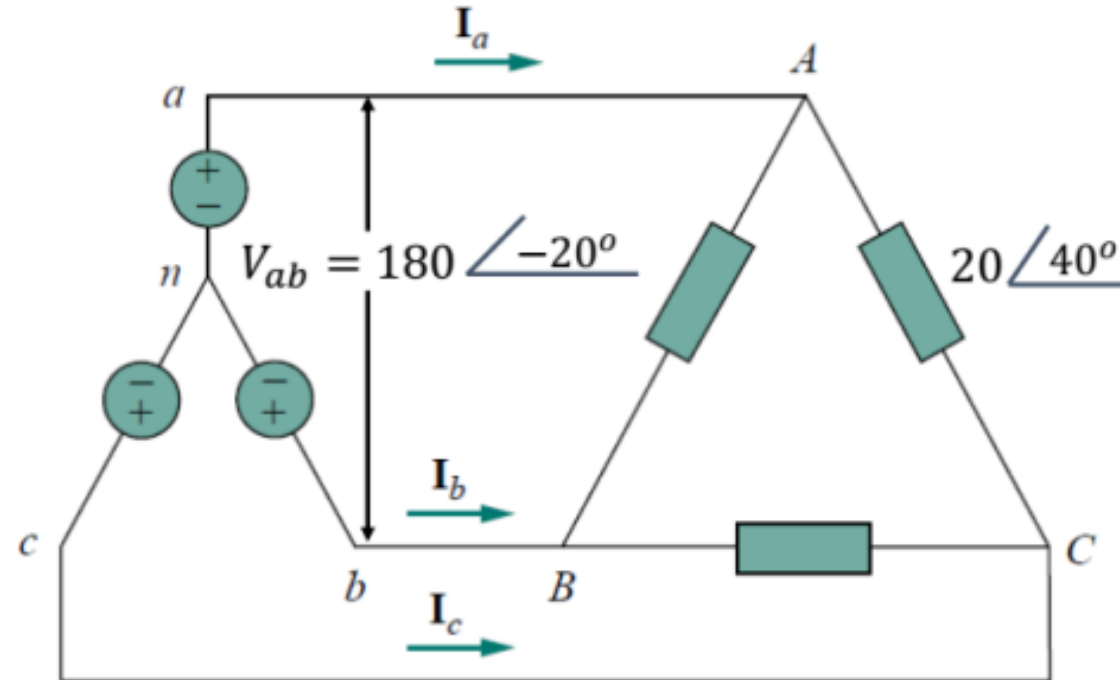One line voltage of a balanced Y-connected source is  $180\angle-20^\circ$ . If the source is connected to a balanced  $\Delta$ -connected load of  $20\angle40^\circ$ . Calculate the (i) phase voltages, (ii) phase currents, (ii) line currents and (iii) complex power at the source and load.



 At Source (Y)

Given

$$V_L = 180 \angle -20^\circ \text{ V}$$

Relationship between phase and line, voltage and current in Y connection

$$\begin{aligned} V_L &= \sqrt{3}V_P \angle 30^\circ \\ I_L &= I_P \end{aligned}$$

(i) phase voltage

$$V_P = \frac{V_L}{\sqrt{3} \angle 30^\circ}$$

$$V_P = \frac{180 \angle -20^\circ}{\sqrt{3} \angle 30^\circ}$$

$$V_P = 103.92 \angle -30^\circ \text{ V}$$

At Load ( $\Delta$ )

Given

$$Z_L = 20 \angle 40^\circ \Omega$$

Relationship between phase and line, voltage and current in  $\Delta$  connection

$$\begin{aligned} I_L &= \sqrt{3}V_P \angle -30^\circ \\ V_L &= V_P \end{aligned}$$

(i) line voltage

Line voltage of load is equal to line voltage of the source

$$V_{AB} = V_{ab} \quad V_L = 180 \angle -20^\circ \text{ V}$$

(ii) phase voltage

$$V_P = V_L = 180 \angle -20^\circ \text{ V}$$

### At Source (Y)

#### (iii) line current

Line current of source is equal to line current of the load

$$I_L = 15.58 \angle -90^\circ \text{ A}$$

#### (ii) Phase current

$$I_P = I_L = 15.58 \angle -90^\circ \text{ A}$$

#### (iii) Complex power

$$S = -(P + jQ)$$

$$S = -(3V_P I_P \cos(\theta_V - \theta_i) + j3V_P I_P \sin(\theta_V - \theta_i))$$

$$= -(3(103.92)(15.58) \cos(-50^\circ + 90^\circ) + j3(103.92)(15.58) \sin(-50^\circ + 90^\circ))$$

$$S = -(3720.847 + j3122.16) \text{ VA}$$

### At Load ( $\Delta$ )

#### (iii) phase current

$$I_P = \frac{V_P}{Z} = \frac{180 \angle -20^\circ}{20 \angle 40^\circ}$$
$$= 9 \angle -60^\circ \text{ A}$$

#### (iii) line current

$$I_L = \sqrt{3} I_P \angle -30^\circ$$

$$I_L = \sqrt{3}(9) \angle -60^\circ \angle -30^\circ$$

$$I_L = 15.58 \angle -90^\circ \text{ A}$$

#### (iii) Complex power

$$S = P + jQ$$

$$S = 3V_P I_P \cos(\theta_V - \theta_i) + j3V_P I_P \sin(\theta_V - \theta_i)$$


$$= 3(180)(9) \cos(-20^\circ + 60^\circ) +$$

$$j3(180)(9) \sin(-20^\circ + 60^\circ)$$

$$S = 3722.98 + j3123.95 \text{ VA}$$



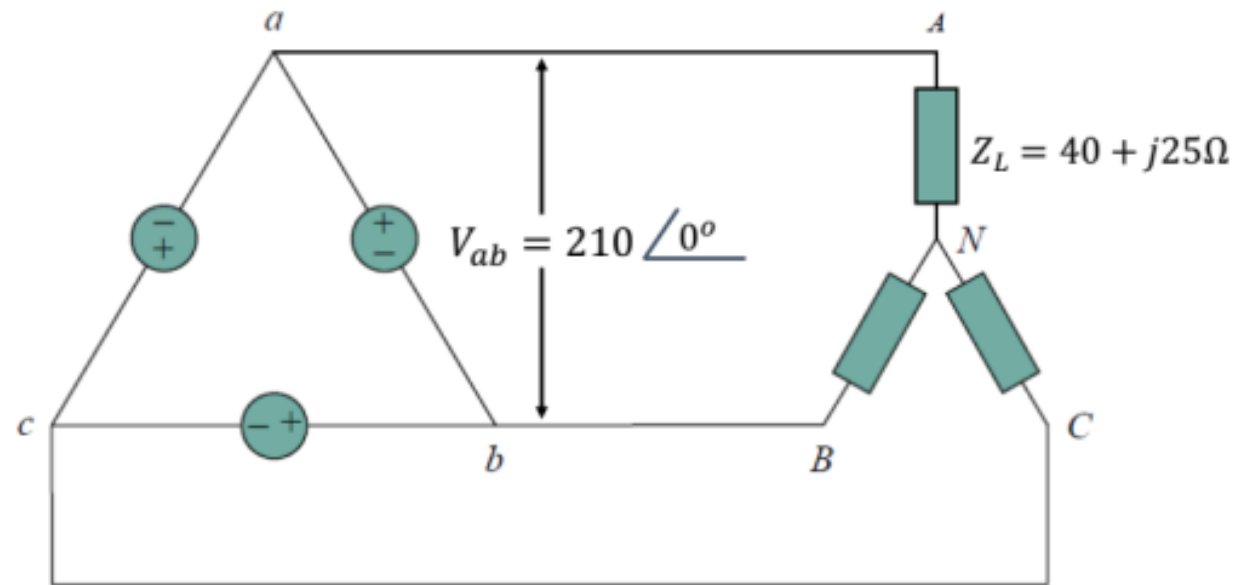A balanced Y-connected load with a phase resistance of  $40\Omega$  and a reactance of  $25\Omega$  is supplied by a balanced  $\Delta$ -connected source with a line voltage of 210 V. Calculate the (i) phase voltages, (ii) phase currents, (ii) line currents and (iii) complex power at the source and load.



### At Source ( $\Delta$ )

#### Given

$$V_L = 210 \angle 0^\circ \text{ V}$$

Relationship between phase and line, voltage and current in  $\Delta$  connection

$$\begin{aligned} I_L &= \sqrt{3}V_P \angle -30^\circ \\ V_L &= V_P \end{aligned}$$

#### (i) phase voltage

$$V_P = V_L = 210 \angle 0^\circ \text{ V}$$

### At Load (Y)

#### Given

$$Z = 40 + j25 \Omega \quad Z_L = 47.17 \angle 32.005^\circ$$

Relationship between phase and line, voltage and current in Y connection

$$\begin{aligned} V_L &= \sqrt{3}V_P \angle 30^\circ \\ I_L &= I_P \end{aligned}$$

#### (i) line voltage

Line voltage of load is equal to line voltage of the source

$$V_{AB} = V_{ab} \quad V_L = 210 \angle 0^\circ \text{ V}$$

#### (ii) phase voltage

$$V_P = \frac{V_L}{\sqrt{3} \angle 30^\circ}$$

$$V_P = 121.24 \angle -30^\circ \text{ V}$$

### At Source ( $\Delta$ )

#### (iii) line current

Line current of source is equal to line current of the load

$$I_L = 2.57 \angle -62.005^\circ \text{ A}$$

#### (ii) Phase current

$$I_P = I_L / (\sqrt{3} \angle -30^\circ)$$

$$I_P = (2.57) / \sqrt{3} \angle -62.005^\circ / 30^\circ$$

$$I_P = 1.483 \angle -32.005^\circ \text{ A}$$

#### (iii) Complex power

$$S = -(P + jQ)$$

$$S = -(3V_P I_P \cos(\theta_V - \theta_i) + j3V_P I_P \sin(\theta_V - \theta_i))$$

$$\begin{aligned} &= -(3(210)(1.483) \cos(0^\circ + 32.005^\circ) + \\ &\quad j3(210)(1.483) \sin(0^\circ + 32.005^\circ)) \end{aligned}$$

$$S = -(792.28 + j495.17) \text{ VA}$$

### At Load (Y)

#### (iii) phase current

$$\begin{aligned} I_P &= \frac{V_P}{Z_L} = \frac{121.24 \angle -30^\circ}{47.17 \angle 32.005^\circ} \\ &= 2.57 \angle -62.005^\circ \text{ A} \end{aligned}$$

#### (iii) line current

$$I_P = I_L = 2.57 \angle -62.005^\circ \text{ A}$$

#### (iii) Complex power

$$S = P + jQ$$

$$S = 3V_P I_P \cos(\theta_V - \theta_i) + j3V_P I_P \sin(\theta_V - \theta_i)$$

$$\begin{aligned} &= 3(121.24)(2.57) \cos(-30^\circ + 62.005^\circ) + \\ &\quad j3(121.24)(2.57) \sin(-30^\circ + 62.005^\circ) \end{aligned}$$

$$S = 792.68 + j495.42 \text{ VA}$$

**Question: Find the real power absorbed by the load for the three-phase circuit shown in Fig.1**

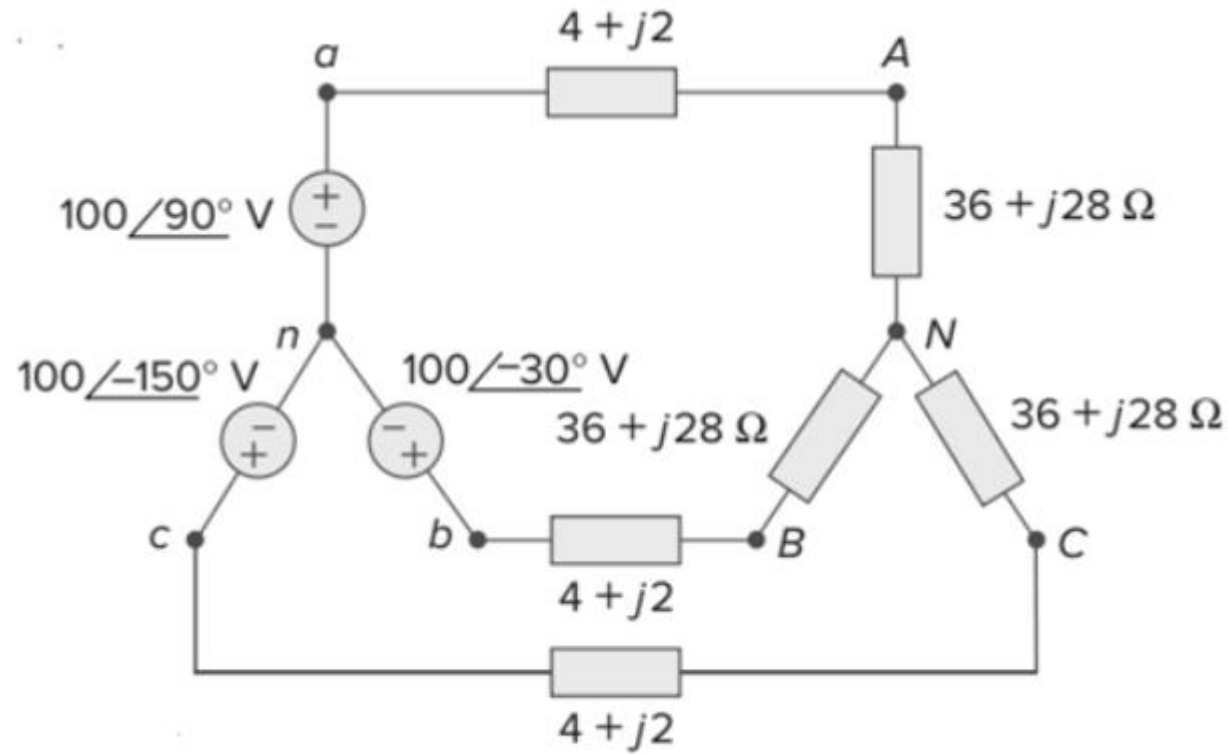


Fig.1

**Question: Find the real power absorbed by the load for the three-phase circuit shown in Fig.1**

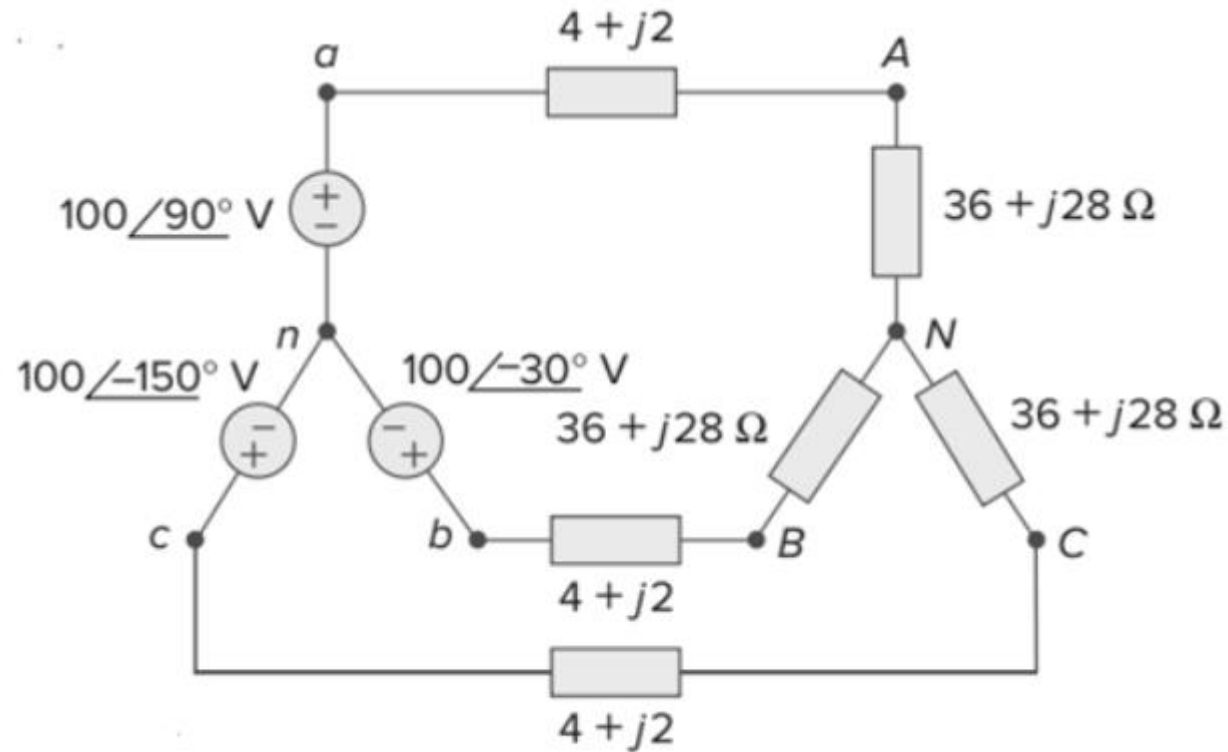


Fig.1

**Answer: 432.02W**